


GPIO LED Control

Since the Raspberry Pi Model B+ (the second version of the Pi 1) the Raspberry Pi has had a 40 Pin header (24 Pins on the very first Pi). These pins provide some very useful functions, but what we are interested in are the GPIO pins that we can turn on and off (some pins have dedicated functions).

An easy way to see if we are actually turning a pin on or off is to use an LED that will light up upon the pin becoming active.

Please be aware, the GPIO pins are 3.3v Logic, and are restricted to 16mA

 Here is a simple circuit of an LED connected to a GPIO Pin.



This is a red LED that has a 2V drop across it, so $3.3\text{v} - 2\text{v} = 1.3\text{v}$. The LED only needs around 5mA, so $R = V/I = 1.3/0.005 = 260\text{ Ohms}$.

When the Pin goes high (under our software control) it will provide 3.3v, and thus the LED will light (famous last words)

If you are using your Raspberry Pi via SSH or a Remote Desktop session, you need to enable remote access of the GPIO Pins, instructions for this are [here](#):

From:
<http://cameraangle.co.uk/> - WalkerWiki - wiki.alanwalker.uk

Permanent link:
http://cameraangle.co.uk/doku.php?id=gpio_led_control&rev=1470763246

Last update: 2023/03/09 22:35

